


1. Sketch waveform for $v_1(t)+v_2(t)$

$$v_1(t) = 10 \sin (\omega t + 20^\circ) \text{ Volts}$$

$$v_2(t) = 5 \sin (\omega t - 45^\circ) \text{ Volts}$$

2. A choke coil having resistor R and inductor L are connected in series with resistance across a 230V, 50Hz AC supply. The circuit draws a current of 5A and lags behind the voltage by 30° . The voltage drop across the resistor is 120V. Calculate phase angle of a choke coil.

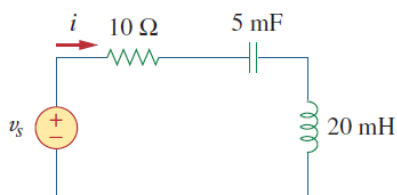3. Find current i in the circuit of Fig. shown below, when $v_s(t) = 50 \cos 200t$ V.




4. For the system of Fig. shown below:

a. Find the total number of watts, volt-amperes reactive, and volt-amperes, and Fp .

b. Find the current I_s .

c. Draw the power triangle.

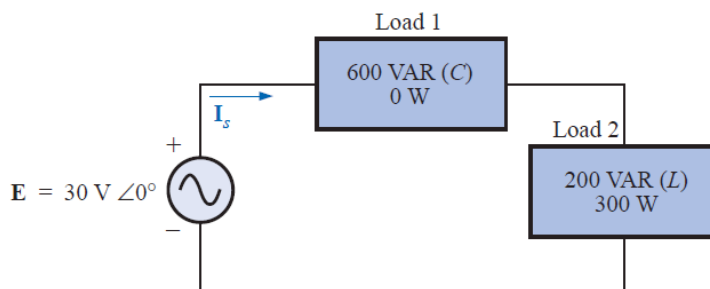

Hint:

$$P_T = 0 + 300 \text{ W} = 300 \text{ W}$$

$$Q_T = 600 \text{ VAR}(C) + 200(L) = 400 \text{ VAR}(C)$$