# Study of the characteristics of PN junction Diode and Zener Diode

**Experiment no. Date:** 

Aim: To study the VI characteristics of PN junction and Zener diodes.

#### **APPARATUS REQUIRED:**


S.No.	Name	Range	Туре	Qty
1	R.P.S			
2	Ammeter			
3	Voltmeter			

#### **COMPONENTS REQUIRED:**


S. No	Name	Range	Туре	Qty
1	zener diode			
2	PN junction diode			
3	Resistor			
4	Bread Board			
	Wires			

#### **Circuit Diagram:**


Forward bias of PN junction diode

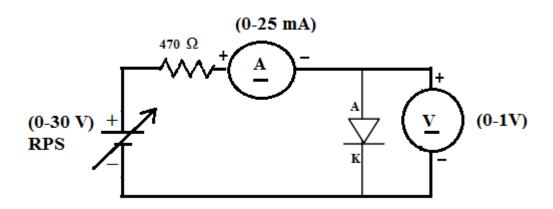

Forward bias of Zener diode

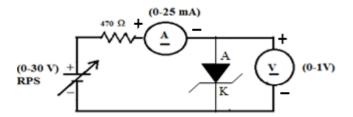


### Reverse bias of Zener diode

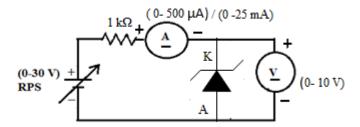


# **Model Graph**
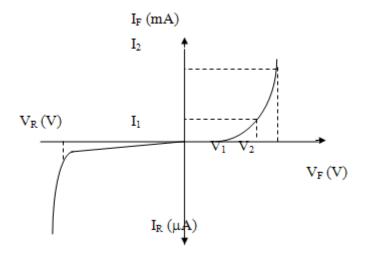
### VI characteristics of PN junction diode



### VI characteristics of Zener diode

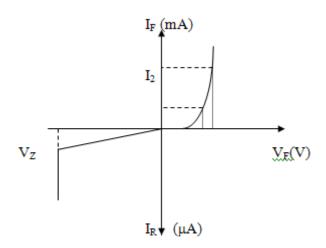

|--|

1. V-I characteristics of PN junction and Zener diode

# Result

Thus, the VI characteristics of PN junction diode and Zener diode were studied.