

EXPT NO. : DESIGN OF HALF ADDER AND FULL ADDER


DATE :

AIM:

To design and simulate half adder and full adder verify the truth table using logic gates.

Tools Used:

LTSPice

 
LOGIC DIAGRAM:**HALF ADDER****TRUTH TABLE:**

A	B	CARRY	SUM
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

LOGIC DIAGRAM:

FULL ADDER

FULL ADDER USING TWO HALF ADDER

 

TRUTH TABLE:

A	B	C	CARRY	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

PROCEDURE:

RESULT: