

change in emitter current ( $\Delta I_E$ ) at constant collector-base voltage ( $V_{CB}$ ) i.e.

$$\text{Input resistance, } r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CB}$$

In fact, input resistance is the opposition offered to the signal current. As a very small  $V_{EB}$  is sufficient to produce a large flow of emitter current  $I_E$ , therefore, input resistance is quite small, of the order of a few ohms.

**2. Output characteristic.** It is the curve between collector current  $I_C$  and collector-base voltage  $V_{CB}$  at \*constant emitter current  $I_E$ . Generally, collector current is taken along y-axis and collector-base voltage along x-axis. Fig. 8.15 shows the output characteristics of a typical transistor in *CB* arrangement.

The following points may be noted from the characteristics :

(i) The collector current  $I_C$  varies with  $V_{CB}$  only at very low voltages ( $< 1\text{ V}$ ). The transistor is *never* operated in this region.

(ii) When the value of  $V_{CB}$  is raised above 1 – 2 V, the collector current becomes constant as indicated by straight horizontal curves. It means that now  $I_C$  is independent of  $V_{CB}$  and depends upon  $I_E$  only. This is consistent with the theory that the emitter current flows *almost* entirely to the collector terminal. The transistor is *always* operated in this region.

(iii) A very large change in collector-base voltage produces only a tiny change in collector current. This means that output resistance is very high.

**Output resistance.** It is the ratio of change in collector-base voltage ( $\Delta V_{CB}$ ) to the resulting change in collector current ( $\Delta I_C$ ) at constant emitter current i.e.

$$\text{Output resistance, } r_o = \frac{\Delta V_{CB}}{\Delta I_C} \text{ at constant } I_E$$

The output resistance of *CB* circuit is very high, of the order of several tens of kilo-ohms. This is not surprising because the collector current changes very slightly with the change in  $V_{CB}$ .

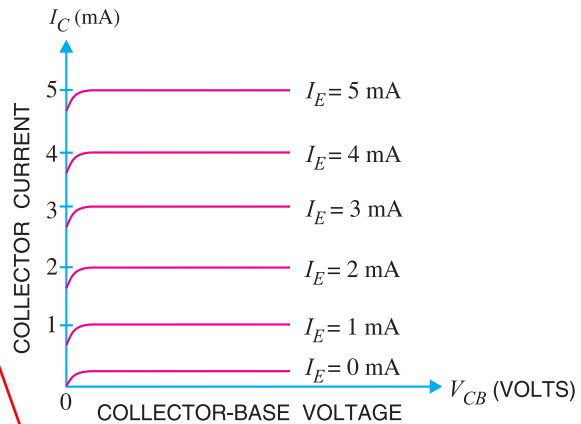


Fig. 8.15

## 8.10 Common Emitter Connection

In this circuit arrangement, input is applied between base and emitter and output is taken from the collector and emitter. Here, emitter of the transistor is common to both input and output circuits and hence the name common emitter connection. Fig. 8.16 (i) shows common emitter *npn* transistor circuit whereas Fig. 8.16 (ii) shows common emitter *pnp* transistor circuit.

\*  $I_E$  has to be kept constant because any change in  $I_E$  will produce corresponding change in  $I_C$ . Here, we are interested to see how  $V_{CB}$  influences  $I_C$ .

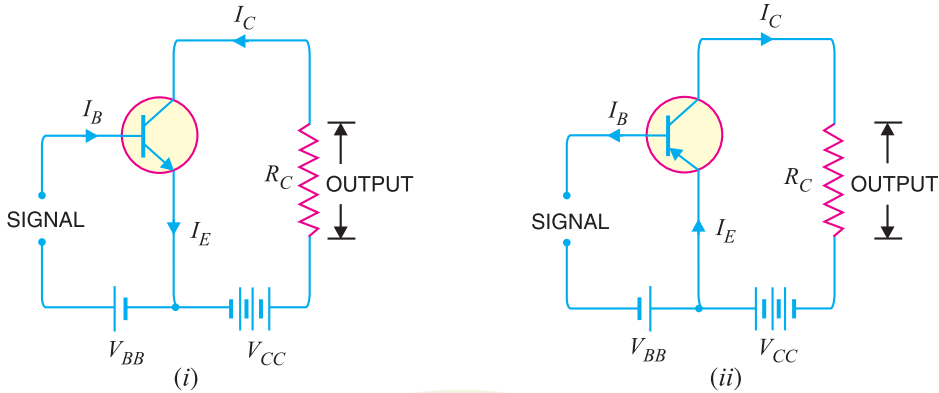


Fig. 8.16

**1. Base current amplification factor ( $\beta$ ).** In common emitter connection, input current is  $I_B$  and output current is  $I_C$ .

The ratio of change in collector current ( $\Delta I_C$ ) to the change in base current ( $\Delta I_B$ ) is known as **base current amplification factor** i.e.

$$\beta^* = \frac{\Delta I_C}{\Delta I_B}$$

In almost any transistor, less than 5% of emitter current flows as the base current. Therefore, the value of  $\beta$  is generally greater than 20. Usually, its value ranges from 20 to 500. This type of connection is frequently used as it gives appreciable current gain as well as voltage gain.

**Relation between  $\beta$  and  $\alpha$ .** A simple relation exists between  $\beta$  and  $\alpha$ . This can be derived as follows :

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \dots(i)$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \dots(ii)$$

Now

$$I_E = I_B + I_C$$

or

$$\Delta I_E = \Delta I_B + \Delta I_C$$

or

$$\Delta I_B = \Delta I_E - \Delta I_C$$

Substituting the value of  $\Delta I_B$  in exp. (i), we get,

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} \quad \dots(iii)$$

Dividing the numerator and denominator of R.H.S. of exp. (iii) by  $\Delta I_E$ , we get,

$$\beta = \frac{\frac{\Delta I_C}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{\alpha}{1 - \alpha} \quad \left[ \because \alpha = \frac{\Delta I_C}{\Delta I_E} \right]$$

$\therefore$

$$\beta = \frac{\alpha}{1 - \alpha}$$

It is clear that as  $\alpha$  approaches unity,  $\beta$  approaches infinity. In other words, the current gain in common emitter connection is very high. It is due to this reason that this circuit arrangement is used in about 90 to 95 percent of all transistor applications.

\* If d.c. values are considered,  $\beta = I_C/I_B$ .

**2. Expression for collector current.** In common emitter circuit,  $I_B$  is the input current and  $I_C$  is the output current.

$$\text{We know } I_E = I_B + I_C \quad \dots(i)$$

$$\text{and } I_C = \alpha I_E + I_{CBO} \quad \dots(ii)$$

$$\text{From exp. (ii), we get, } I_C = \alpha I_E + I_{CBO} = \alpha (I_B + I_C) + I_{CBO}$$

$$\text{or } I_C (1 - \alpha) = \alpha I_B + I_{CBO}$$

$$\text{or } I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO} \quad \dots(iii)$$

From exp. (iii), it is apparent that if  $I_B = 0$  (i.e. base circuit is open), the collector current will be the current to the emitter. This is abbreviated as  $I_{CEO}$ , meaning collector-emitter current with base open.


$$\therefore I_{CEO} = \frac{1}{1 - \alpha} I_{CBO}$$

Substituting the value of  $\frac{1}{1 - \alpha} I_{CBO} = I_{CEO}$  in exp. (iii), we get,

$$I_C = \frac{\alpha}{1 - \alpha} I_B + I_{CEO}$$

$$\text{or } I_C = \beta I_B + I_{CEO} \quad \left( \because \beta = \frac{\alpha}{1 - \alpha} \right)$$

**Concept of  $I_{CEO}$ .** In CE configuration, a small collector current flows even when the base current is zero [See Fig. 8.17 (i)]. This is the collector cut off current (i.e. the collector current that flows when base is open) and is denoted by  $I_{CEO}$ . The value of  $I_{CEO}$  is much larger than  $I_{CBO}$ .

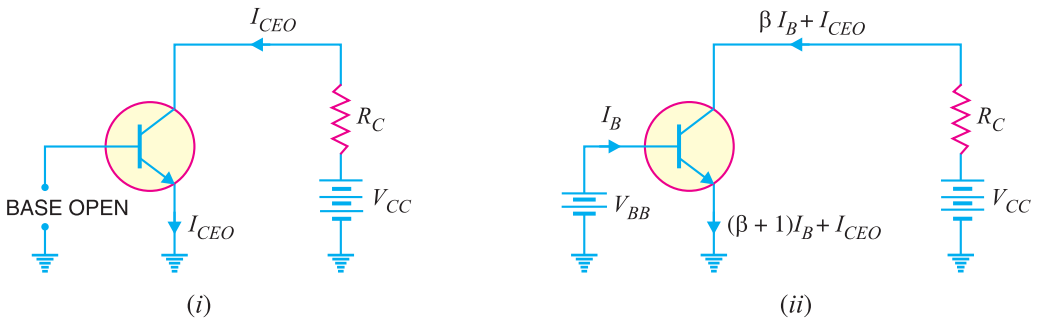

**Fig. 8.17**

When the base voltage is applied as shown in Fig. 8.17 (ii), then the various currents are :

$$\text{Base current} = I_B$$

$$\text{Collector current} = \beta I_B + I_{CEO}$$

$$\text{Emitter current} = \text{Collector current} + \text{Base current}$$

$$= (\beta I_B + I_{CEO}) + I_B = (\beta + 1) I_B + I_{CEO}$$

It may be noted here that :

$$I_{CEO} = \frac{1}{1 - \alpha} I_{CBO} = (\beta + 1) I_{CBO} \quad \left[ \because \frac{1}{1 - \alpha} = \beta + 1 \right]$$

## 8.11. Measurement of Leakage Current

A very small leakage current flows in all transistor circuits. However, in most cases, it is quite small and can be neglected.

**(i) Circuit for  $I_{CEO}$  test.** Fig. 8.18 shows the circuit for measuring  $I_{CEO}$ . Since base is open

( $I_B = 0$ ), the transistor is in cut off. Ideally,  $I_C = 0$  but actually there is a small current from collector to emitter due to minority carriers. It is called  $I_{CEO}$  (collector-to-emitter current with base open). This current is usually in the nA range for silicon. A faulty transistor will often have excessive leakage current.

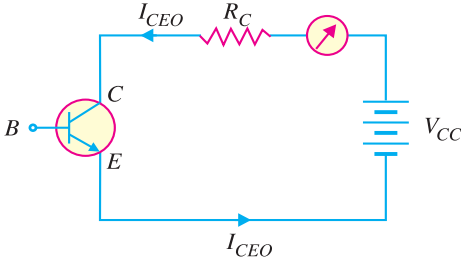


Fig. 8.18

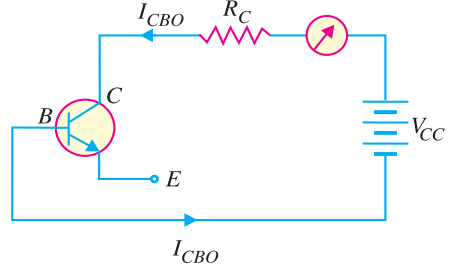


Fig. 8.19

**(ii) Circuit for  $I_{CBO}$  test.** Fig. 8.19 shows the circuit for measuring  $I_{CBO}$ . Since the emitter is open ( $I_E = 0$ ), there is a small current from collector to base. This is called  $I_{CBO}$  (collector-to-base current with emitter open). This current is due to the movement of minority carriers across base-collector junction. The value of  $I_{CBO}$  is also small. If in measurement,  $I_{CBO}$  is excessive, then there is a possibility that collector-base is shorted.

**Example 8.8.** Find the value of  $\beta$  if (i)  $\alpha = 0.9$  (ii)  $\alpha = 0.98$  (iii)  $\alpha = 0.99$ .

**Solution.** (i) 
$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.9}{1 - 0.9} = 9$$

(ii) 
$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

(iii) 
$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.99}{1 - 0.99} = 99$$

**Example 8.9.** Calculate  $I_E$  in a transistor for which  $\beta = 50$  and  $I_B = 20 \mu\text{A}$ .

**Solution.** Here  $\beta = 50$ ,  $I_B = 20 \mu\text{A} = 0.02 \text{ mA}$

Now 
$$\beta = \frac{I_C}{I_B}$$

$\therefore I_C = \beta I_B = 50 \times 0.02 = 1 \text{ mA}$

Using the relation,  $I_E = I_B + I_C = 0.02 + 1 = 1.02 \text{ mA}$

**Example 8.10.** Find the  $\alpha$  rating of the transistor shown in Fig. 8.20. Hence determine the value of  $I_C$  using both  $\alpha$  and  $\beta$  rating of the transistor.

**Solution.** Fig. 8.20 shows the conditions of the problem.

$$\alpha = \frac{\beta}{1 + \beta} = \frac{49}{1 + 49} = 0.98$$

The value of  $I_C$  can be found by using either  $\alpha$  or  $\beta$  rating as under :

$$I_C = \alpha I_E = 0.98 (12 \text{ mA}) = 11.76 \text{ mA}$$

Also 
$$I_C = \beta I_B = 49 (240 \mu\text{A}) = 11.76 \text{ mA}$$

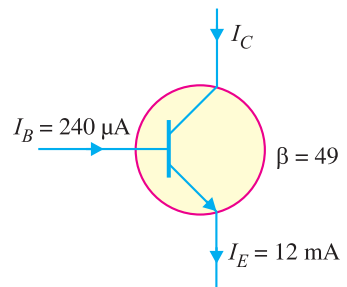


Fig. 8.20

**Example 8.11.** For a transistor,  $\beta = 45$  and voltage drop across  $1\text{ k}\Omega$  which is connected in the collector circuit is 1 volt. Find the base current for common emitter connection.

**Solution.** Fig. 8.21 shows the required common emitter connection. The voltage drop across  $R_C (= 1\text{ k}\Omega)$  is 1 volt.

$$\therefore I_C = \frac{1\text{ V}}{1\text{ k}\Omega} = 1\text{ mA}$$

$$\text{Now } \beta = \frac{I_C}{I_B}$$

$$\therefore I_B = \frac{I_C}{\beta} = \frac{1}{45} = 0.022\text{ mA}$$

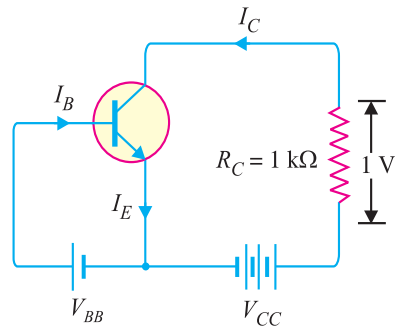


Fig. 8.21

**Example 8.12.** A transistor is connected in common emitter (CE) configuration in which collector supply is 8V and the voltage drop across resistance  $R_C$  connected in the collector circuit is 0.5V. The value of  $R_C = 800\ \Omega$ . If  $\alpha = 0.96$ , determine :

- collector-emitter voltage
- base current

**Solution.** Fig. 8.22 shows the required common emitter connection with various values.

(i) Collector-emitter voltage,

$$V_{CE} = V_{CC} - 0.5 = 8 - 0.5 = 7.5\text{ V}$$

(ii) The voltage drop across  $R_C (= 800\ \Omega)$  is 0.5 V.

$$\therefore I_C = \frac{0.5\text{ V}}{800\ \Omega} = \frac{5}{8}\text{ mA} = 0.625\text{ mA}$$

$$\text{Now } \beta = \frac{\alpha}{1 - \alpha} = \frac{0.96}{1 - 0.96} = 24$$

$$\therefore \text{Base current, } I_B = \frac{I_C}{\beta} = \frac{0.625}{24} = 0.026\text{ mA}$$



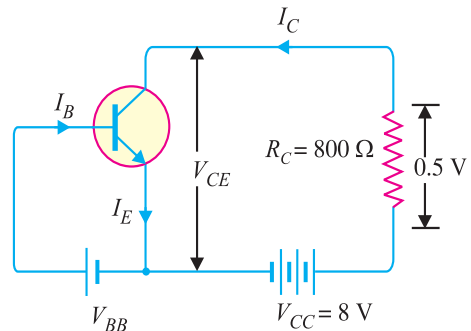


Fig. 8.22

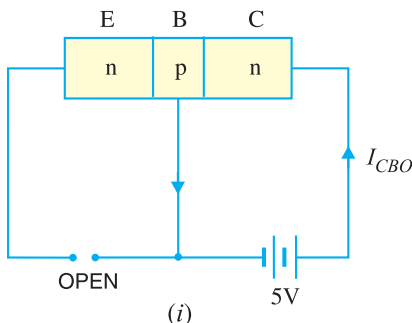**Example 8.13.** An n-p-n transistor at room temperature has its emitter disconnected. A voltage of 5V is applied between collector and base. With collector positive, a current of  $0.2\ \mu\text{A}$  flows. When the base is disconnected and the same voltage is applied between collector and emitter, the current is found to be  $20\ \mu\text{A}$ . Find  $\alpha$ ,  $I_E$  and  $I_B$  when collector current is 1mA.



(i)

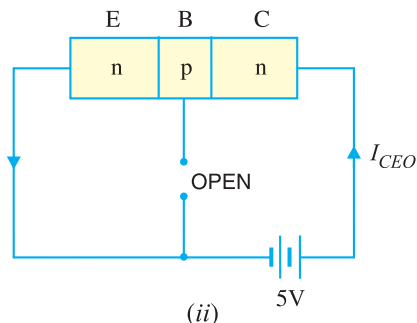

(ii)

Fig. 8.23

**Solution.** When the emitter circuit is open [See Fig. 8.23 (i)], the collector-base junction is reverse biased. A small leakage current  $I_{CBO}$  flows due to minority carriers.

$$\therefore I_{CBO} = 0.2 \mu\text{A} \quad \dots \text{given}$$

When base is open [See Fig. 8.23 (ii)], a small leakage current  $I_{CEO}$  flows due to minority carriers.

$$\therefore I_{CEO} = 20 \mu\text{A} \quad \dots \text{given}$$

We know 
$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha}$$

or 
$$20 = \frac{0.2}{1 - \alpha}$$

$$\therefore \alpha = 0.99$$

Now 
$$I_C = \alpha I_E + I_{CBO}$$

Here 
$$I_C = 1\text{mA} = 1000 \mu\text{A}; \alpha = 0.99; I_{CBO} = 0.2 \mu\text{A}$$

$$\therefore 1000 = 0.99 \times I_E + 0.2$$

or 
$$I_E = \frac{1000 - 0.2}{0.99} = 1010 \mu\text{A}$$

and 
$$I_B = I_E - I_C = 1010 - 1000 = 10 \mu\text{A}$$

**Example 8.14.** The collector leakage current in a transistor is  $300 \mu\text{A}$  in CE arrangement. If now the transistor is connected in CB arrangement, what will be the leakage current? Given that  $\beta = 120$ .

**Solution.** 
$$I_{CEO} = 300 \mu\text{A}$$

$$\beta = 120; \alpha = \frac{\beta}{\beta + 1} = \frac{120}{120 + 1} = 0.992$$

Now, 
$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha}$$

$$\therefore I_{CBO} = (1 - \alpha) I_{CEO} = (1 - 0.992) \times 300 = 2.4 \mu\text{A}$$

Note that leakage current in CE arrangement (i.e.  $I_{CEO}$ ) is much more than in CB arrangement (i.e.  $I_{CBO}$ ).

**Example 8.15.** For a certain transistor,  $I_B = 20 \mu\text{A}$ ;  $I_C = 2 \text{mA}$  and  $\beta = 80$ . Calculate  $I_{CBO}$ .

**Solution.**

$$I_C = \beta I_B + I_{CEO}$$

or 
$$2 = 80 \times 0.02 + I_{CEO}$$

$$\therefore I_{CEO} = 2 - 80 \times 0.02 = 0.4 \text{mA}$$

Now 
$$\alpha = \frac{\beta}{\beta + 1} = \frac{80}{80 + 1} = 0.988$$

$$\therefore I_{CBO} = (1 - \alpha) I_{CEO} = (1 - 0.988) \times 0.4 = 0.0048 \text{mA}$$

**Example 8.16.** Using diagrams, explain the correctness of the relation  $I_{CEO} = (\beta + 1) I_{CBO}$ .

**Solution.** The leakage current  $I_{CBO}$  is the current that flows through the base-collector junction when emitter is open as shown in Fig. 8.24. When the transistor is in CE arrangement, the \*base current (i.e.  $I_{CBO}$ ) is multiplied by  $\beta$  in the collector as shown in Fig. 8.25.

$$\therefore I_{CEO} = I_{CBO} + \beta I_{CBO} = (\beta + 1) I_{CBO}$$

\* The current  $I_{CBO}$  is amplified because it is forced to flow across the base-emitter junction.

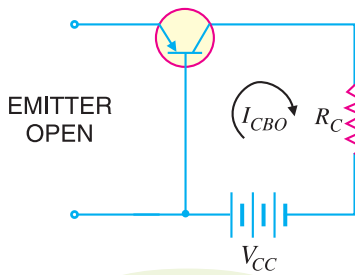


Fig. 8.24

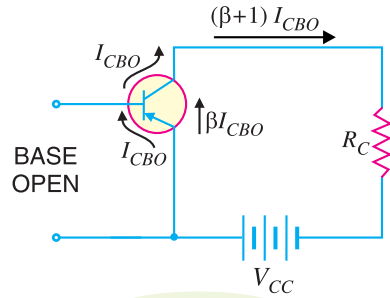


Fig. 8.25

**Example 8.17** Determine  $V_{CB}$  in the transistor \* circuit shown in Fig. 8.26 (i). The transistor is of silicon and has  $\beta = 150$ .

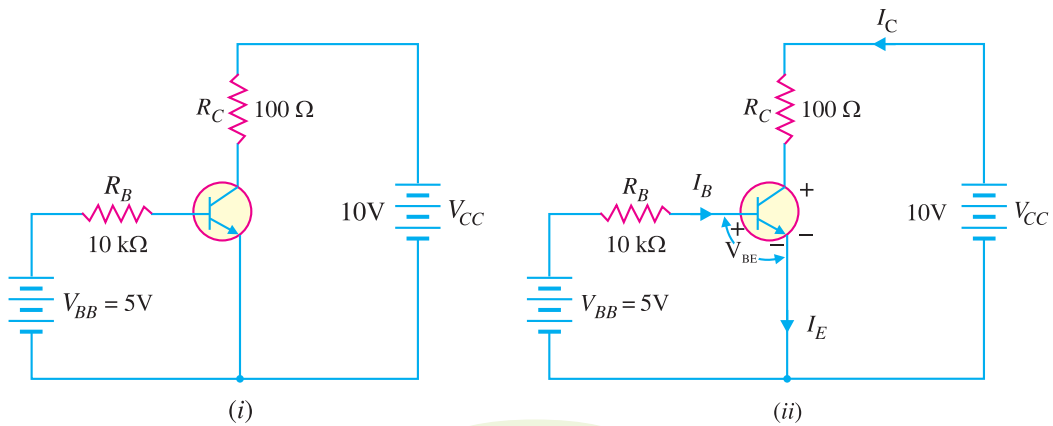


Fig. 8.26

**Solution.** Fig. 8.26 (i) shows the transistor circuit while Fig. 8.26 (ii) shows the various currents and voltages along with polarities.

Applying Kirchhoff's voltage law to base-emitter loop, we have,

$$V_{BB} - I_B R_B - V_{BE} = 0$$

$$\text{or} \quad I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5\text{V} - 0.7\text{V}}{10\text{ k}\Omega} = 430\text{ }\mu\text{A}$$

$$\therefore I_C = \beta I_B = (150)(430\text{ }\mu\text{A}) = 64.5\text{ mA}$$

$$\begin{aligned} \text{Now} \quad V_{CE} &= V_{CC} - I_C R_C \\ &= 10\text{V} - (64.5\text{ mA})(100\Omega) = 10\text{V} - 6.45\text{V} = 3.55\text{V} \end{aligned}$$

$$\text{We know that : } V_{CE} = V_{CB} + V_{BE}$$

$$\therefore V_{CB} = V_{CE} - V_{BE} = 3.55 - 0.7 = \mathbf{2.85\text{V}}$$

**Example 8.18.** In a transistor,  $I_B = 68\text{ }\mu\text{A}$ ,  $I_E = 30\text{ mA}$  and  $\beta = 440$ . Determine the  $\alpha$  rating of the transistor. Then determine the value of  $I_C$  using both the  $\alpha$  rating and  $\beta$  rating of the transistor.

**Solution.**

$$\alpha = \frac{\beta}{\beta + 1} = \frac{440}{440 + 1} = \mathbf{0.9977}$$

\* The resistor  $R_B$  controls the base current  $I_B$  and hence collector current  $I_C$  ( $= \beta I_B$ ). If  $R_B$  is increased, the base current ( $I_B$ ) decreases and hence collector current ( $I_C$ ) will decrease and vice-versa.

$$I_C = \alpha I_E = (0.9977) (30 \text{ mA}) = \mathbf{29.93 \text{ mA}}$$

Also

$$I_C = \beta I_B = (440) (68 \mu\text{A}) = \mathbf{29.93 \text{ mA}}$$


**Example 8.19.** A transistor has the following ratings :  $I_{C(\text{max})} = 500 \text{ mA}$  and  $\beta_{\text{max}} = 300$ . Determine the maximum allowable value of  $I_B$  for the device.

**Solution.**

$$I_{B(\text{max})} = \frac{I_{C(\text{max})}}{\beta_{\text{max}}} = \frac{500 \text{ mA}}{300} = \mathbf{1.67 \text{ mA}}$$

For this transistor, if the base current is allowed to exceed 1.67 mA, the collector current will exceed its maximum rating of 500 mA and the transistor will probably be destroyed.

**Example 8.20.** Fig. 8.27 shows the open circuit failures in a transistor. What will be the circuit behaviour in each case ?

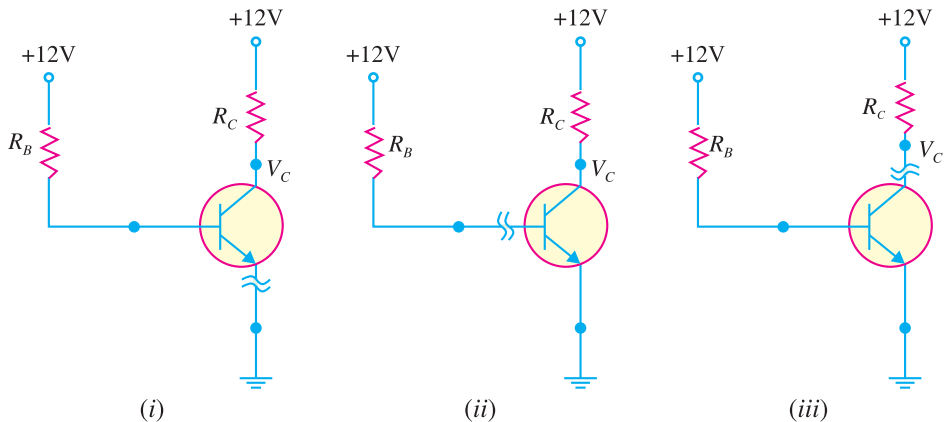

**Fig. 8.27**

**Solution.** \*Fig 8.27 shows the open circuit failures in a transistor. We shall discuss the circuit behaviour in each case.

**(i) Open emitter.** Fig. 8.27 (i) shows an open emitter failure in a transistor. Since the collector diode is not forward biased, it is **OFF** and there can be neither collector current nor base current. Therefore, there will be no voltage drops across either resistor and the voltage at the base and at the collector leads of the transistor will be 12V.

**(ii) Open-base.** Fig. 8.27 (ii) shows an open base failure in a transistor. Since the base is open, there can be no base current so that the transistor is in **cut-off**. Therefore, all the transistor currents are 0A. In this case, the base and collector voltages will both be at 12V.

**Note.** It may be noted that an open failure at either the base or emitter will produce similar results.

**(iii) Open collector.** Fig. 8.27 (iii) shows an open collector failure in a transistor. In this case, the emitter diode is still **ON**, so we expect to see 0.7V at the base. However, we will see 12V at the collector because there is no collector current.

**Example 8.21.** Fig. 8.28 shows the short circuit failures in a transistor. What will be the circuit behaviour in each case ?

\* The collector resistor  $R_C$  controls the collector voltage  $V_C (= V_{CC} - I_C R_C)$ . When  $R_C$  increases,  $V_C$  decreases and vice-versa.



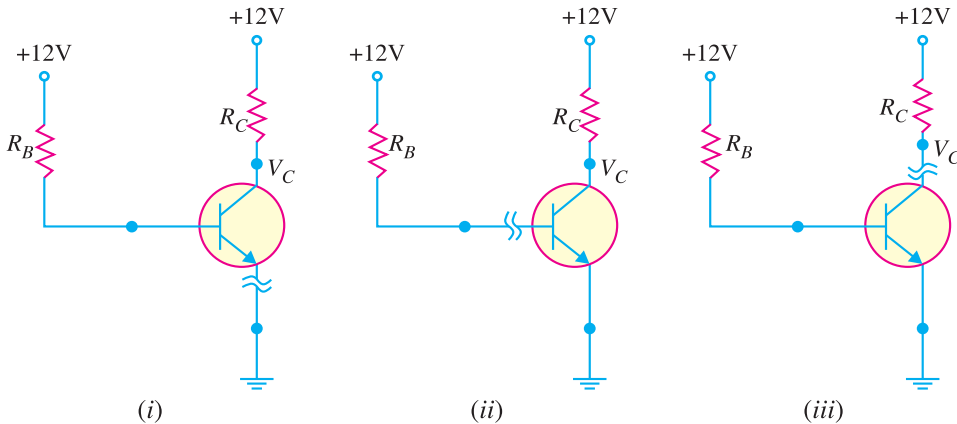


Fig. 8.28

**Solution.** Fig. 8.28 shows the short circuit failures in a transistor. We shall discuss the circuit behaviour in each case.

**(i) Collector-emitter short.** Fig. 8.28 (i) shows a short between collector and emitter. The emitter diode is still forward biased, so we expect to see 0.7V at the base. Since the collector is shorted to the emitter,  $V_C = V_E = 0V$ .

**(ii) Base-emitter short.** Fig. 8.28 (ii) shows a short between base and emitter. Since the base is now directly connected to ground,  $V_B = 0$ . Therefore, the current through  $R_B$  will be diverted to ground and there is no current to forward bias the emitter diode. As a result, the transistor will be *cut-off* and there is no collector current. So we will expect the collector voltage to be 12V.

**(iii) Collector-base short.** Fig. 8.28 (iii) shows a short between the collector and the base. In this case, the emitter diode is still forward biased so  $V_B = 0.7V$ . Now, however, because the collector is shorted to the base,  $V_C = V_B = 0.7V$ .

**Note.** The collector-emitter short is probably the most common type of fault in a transistor. It is because the collector current ( $I_C$ ) and collector-emitter voltage ( $V_{CE}$ ) are responsible for the major part of the power dissipation in the transistor. As we shall see (See Art. 8.23), the power dissipation in a transistor is mainly due to  $I_C$  and  $V_{CE}$  (i.e.  $P_D = V_{CE} I_C$ ). Therefore, the transistor chip between the collector and the emitter is most likely to melt first.

## 8.12 Characteristics of Common Emitter Connection

The important characteristics of this circuit arrangement are the *input characteristics* and *output characteristics*.

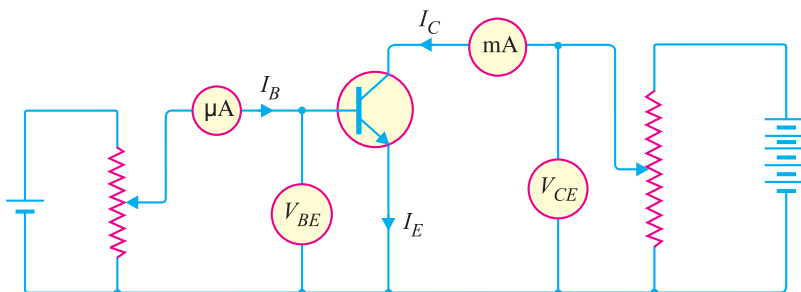


Fig. 8.29

**1. Input characteristic.** It is the curve between base current  $I_B$  and base-emitter voltage  $V_{BE}$  at constant collector-emitter voltage  $V_{CE}$ .

The input characteristics of a  $CE$  connection can be determined by the circuit shown in Fig. 8.29. Keeping  $V_{CE}$  constant (say at 10 V), note the base current  $I_B$  for various values of  $V_{BE}$ . Then plot the readings obtained on the graph, taking  $I_B$  along y-axis and  $V_{BE}$  along x-axis. This gives the input characteristic at  $V_{CE} = 10\text{V}$  as shown in Fig. 8.30. Following a similar procedure, a family of input characteristics can be drawn. The following points may be noted from the characteristics :

(i) The characteristic resembles that of a forward biased diode curve. This is expected since the base-emitter section of transistor is a diode and it is forward biased.

(ii) As compared to  $CB$  arrangement,  $I_B$  increases less rapidly with  $V_{BE}$ . Therefore, input resistance of a  $CE$  circuit is higher than that of  $CB$  circuit.

**Input resistance.** It is the ratio of change in base-emitter voltage ( $\Delta V_{BE}$ ) to the change in base current ( $\Delta I_B$ ) at constant  $V_{CE}$  i.e.

$$\text{Input resistance, } r_i = \frac{\Delta V_{BE}}{\Delta I_B} \text{ at constant } V_{CE}$$

The value of input resistance for a  $CE$  circuit is of the order of a few hundred ohms.

**2. Output characteristic.** It is the curve between collector current  $I_C$  and collector-emitter voltage  $V_{CE}$  at constant base current  $I_B$ .

The output characteristics of a  $CE$  circuit can be drawn with the help of the circuit shown in Fig. 8.29. Keeping the base current  $I_B$  fixed at some value say,  $5\text{ }\mu\text{A}$ , note the collector current  $I_C$  for various values of  $V_{CE}$ . Then plot the readings on a graph, taking  $I_C$  along y-axis and  $V_{CE}$  along x-axis. This gives the output characteristic at  $I_B = 5\text{ }\mu\text{A}$  as shown in Fig. 8.31 (i). The test can be repeated for  $I_B = 10\text{ }\mu\text{A}$  to obtain the new output characteristic as shown in Fig. 8.31 (ii). Following similar procedure, a family of output characteristics can be drawn as shown in Fig. 8.31 (iii).

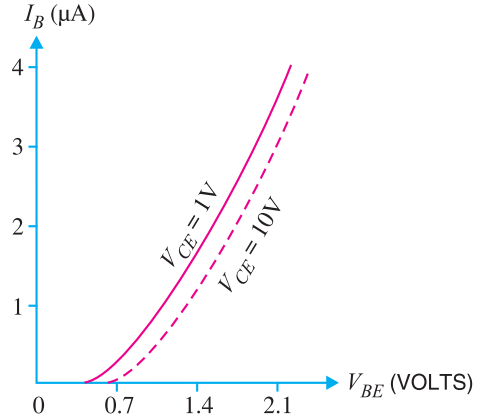


Fig. 8.30

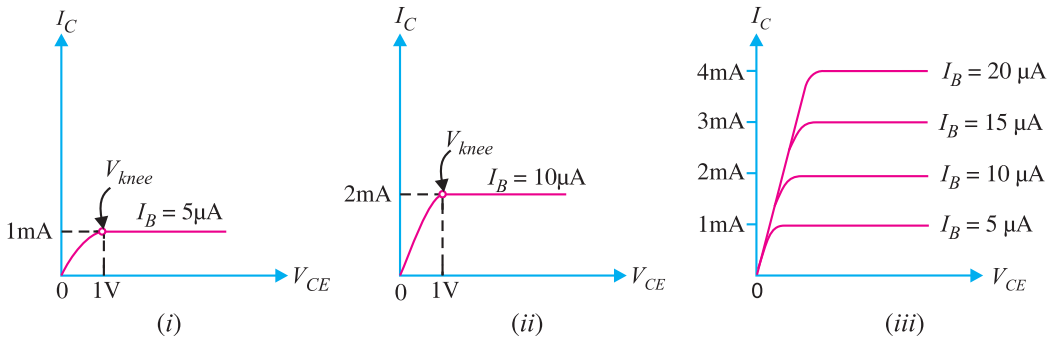


Fig. 8.31

The following points may be noted from the characteristics:

(i) The collector current  $I_C$  varies with  $V_{CE}$  for  $V_{CE}$  between 0 and 1V only. After this, collector current becomes *almost* constant and independent of  $V_{CE}$ . This value of  $V_{CE}$  upto which collector

## 162 ■ Principles of Electronics

current  $I_C$  changes with  $V_{CE}$  is called the **knee voltage** ( $V_{knee}$ ). *The transistors are always operated in the region above knee voltage.*

(ii) Above knee voltage,  $I_C$  is almost constant. However, a small increase in  $I_C$  with increasing  $V_{CE}$  is caused by the collector depletion layer getting wider and capturing a few more majority carriers before electron-hole combinations occur in the base area.

(iii) For any value of  $V_{CE}$  above knee voltage, the collector current  $I_C$  is approximately equal to  $\beta \times I_B$ .

**Output resistance.** It is the ratio of change in collector-emitter voltage ( $\Delta V_{CE}$ ) to the change in collector current ( $\Delta I_C$ ) at constant  $I_B$  i.e.

$$\text{Output resistance, } r_o = \frac{\Delta V_{CE}}{\Delta I_C} \text{ at constant } I_B$$

It may be noted that whereas the output characteristics of *CB* circuit are horizontal, they have noticeable slope for the *CE* circuit. Therefore, the output resistance of a *CE* circuit is less than that of *CB* circuit. Its value is of the order of 50 k $\Omega$ .

### 8.13 Common Collector Connection

In this circuit arrangement, input is applied between base and collector while output is taken between the emitter and collector. Here, collector of the transistor is common to both input and output circuits and hence the name common collector connection. Fig. 8.32 (i) shows common collector *npn* transistor circuit whereas Fig. 8.32 (ii) shows common collector *pnp* circuit.

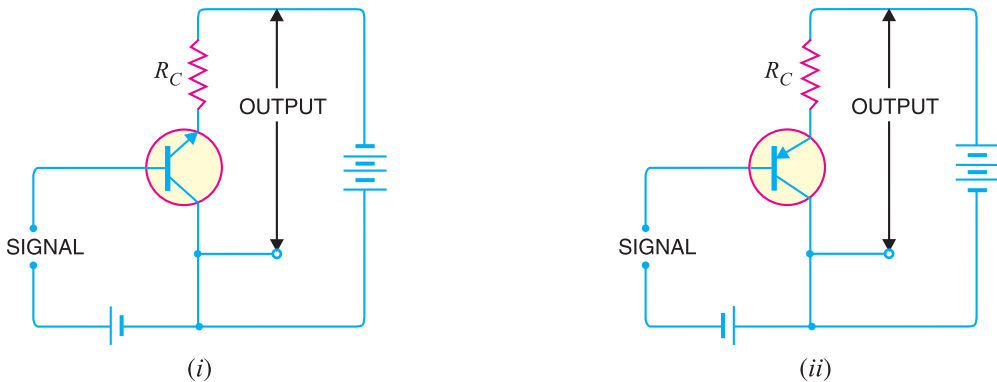


Fig. 8.32

(i) **Current amplification factor  $\gamma$ .** In common collector circuit, input current is the base current  $I_B$  and output current is the emitter current  $I_E$ . Therefore, current amplification in this circuit arrangement can be defined as under :

*The ratio of change in emitter current ( $\Delta I_E$ ) to the change in base current ( $\Delta I_B$ ) is known as **current amplification factor** in common collector (CC) arrangement i.e.*

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

This circuit provides about the same current gain as the common emitter circuit as  $\Delta I_E \simeq \Delta I_C$ . However, its voltage gain is always less than 1.

**Relation between  $\gamma$  and  $\alpha$**

$$\gamma = \frac{\Delta I_E}{\Delta I_B} \quad \dots(i)$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \dots(ii)$$

$$\text{Now} \quad I_E = I_B + I_C$$

$$\text{or} \quad \Delta I_E = \Delta I_B + \Delta I_C$$

$$\text{or} \quad \Delta I_B = \Delta I_E - \Delta I_C$$

Substituting the value of  $\Delta I_B$  in exp. (i), we get,

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

Dividing the numerator and denominator of R.H.S. by  $\Delta I_E$ , we get,

$$\gamma = \frac{\frac{\Delta I_E}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{1}{1 - \alpha} \quad \left( \alpha = \frac{\Delta I_C}{\Delta I_E} \right)$$

$$\therefore \gamma = \frac{1}{1 - \alpha}$$

### (ii) Expression for collector current

$$\text{We know} \quad I_C = \alpha I_E + I_{CBO} \quad (\text{See Art. 8.8})$$

$$\text{Also} \quad I_E = I_B + I_C = I_B + (\alpha I_E + I_{CBO})$$

$$\therefore I_E (1 - \alpha) = I_B + I_{CBO}$$

$$\text{or} \quad I_E = \frac{I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

$$\text{or} \quad I_C = \alpha I_E + I_{CBO} = \alpha \left( \frac{I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha} \right) + I_{CBO}$$

**(iii) Applications.** The common collector circuit has very high input resistance (about 750 k $\Omega$ ) and very low output resistance (about 25  $\Omega$ ). Due to this reason, the voltage gain provided by this circuit is always less than 1. Therefore, this circuit arrangement is seldom used for amplification. However, due to relatively high input resistance and low output resistance, this circuit is primarily used for impedance matching *i.e.* for driving a low impedance load from a high impedance source.

## 8.14 Comparison of Transistor Connections

The comparison of various characteristics of the three connections is given below in the tabular form.

S. No.	Characteristic	Common base	Common emitter	Common collector
1.	Input resistance	Low (about 100 $\Omega$ )	Low (about 750 $\Omega$ )	Very high (about 750 k $\Omega$ )
2.	Output resistance	Very high (about 450 k $\Omega$ )	High (about 45 k $\Omega$ )	Low (about 50 $\Omega$ )
3.	Voltage gain	about 150	about 500	less than 1
4.	Applications	For high frequency applications	For audio frequency applications	For impedance matching
5.	Current gain	No (less than 1)	High ( $\beta$ )	Appreciable

The following points are worth noting about transistor arrangements :

$$* \quad \beta = \frac{\alpha}{1 - \alpha} \quad \therefore \quad \beta + 1 = \frac{\alpha}{1 - \alpha} + 1 = \frac{1}{1 - \alpha}$$

**(i) CB Circuit.** The input resistance ( $r_i$ ) of *CB* circuit is low because  $I_E$  is high. The output resistance ( $r_o$ ) is high because of reverse voltage at the collector. It has no current gain ( $\alpha < 1$ ) but voltage gain can be high. The *CB* circuit is seldom used. The only advantage of *CB* circuit is that it provides good stability against increase in temperature.

**(ii) CE Circuit.** The input resistance ( $r_i$ ) of a *CE* circuit is high because of small  $I_B$ . Therefore,  $r_i$  for a *CE* circuit is much higher than that of *CB* circuit. The output resistance ( $r_o$ ) of *CE* circuit is smaller than that of *CB* circuit. The current gain of *CE* circuit is large because  $I_C$  is much larger than  $I_B$ . The voltage gain of *CE* circuit is larger than that of *CB* circuit. The *CE* circuit is generally used because it has the best combination of voltage gain and current gain. The disadvantage of *CE* circuit is that the leakage current is amplified in the circuit, but bias stabilisation methods can be used.

**(iii) CC Circuit.** The input resistance ( $r_i$ ) and output resistance ( $r_o$ ) of *CC* circuit are respectively high and low as compared to other circuits. There is no voltage gain ( $A_v < 1$ ) in a *CC* circuit. This circuit is often used for impedance matching.

## 8.15 Commonly Used Transistor Connection

Out of the three transistor connections, the common emitter circuit is the most efficient. It is used in about 90 to 95 per cent of all transistor applications. The main reasons for the widespread use of this circuit arrangement are :

**(i) High current gain.** In a common emitter connection,  $I_C$  is the output current and  $I_B$  is the input current. In this circuit arrangement, collector current is given by :

$$I_C = \beta I_B + I_{CEO}$$

As the value of  $\beta$  is very large, therefore, the output current  $I_C$  is much more than the input current  $I_B$ . Hence, the current gain in *CE* arrangement is very high. It may range from 20 to 500.

**(ii) High voltage and power gain.** Due to high current gain, the common emitter circuit has the highest voltage and power gain of three transistor connections. This is the major reason for using the transistor in this circuit arrangement.

**(iii) Moderate output to input impedance ratio.** In a common emitter circuit, the ratio of output impedance to input impedance is small (about 50). This makes this circuit arrangement an ideal one for coupling between various transistor stages. However, in other connections, the ratio of output impedance to input impedance is very large and hence coupling becomes highly inefficient due to gross mismatching.

## 8.16 Transistor as an Amplifier in CE Arrangement

Fig. 8.33 shows the common emitter *npn* amplifier circuit. Note that a battery  $V_{BB}$  is connected in the input circuit in addition to the signal voltage. This d.c. voltage is known as *bias voltage* and its magnitude is such that it always keeps the emitter-base junction forward \*biased regardless of the polarity of the signal source.

**Operation.** During the positive half-cycle of the \*\*signal, the forward bias across the emitter-base junction is increased. Therefore, more electrons flow from the emitter to the collector *via* the base. This causes an increase in collector current. The increased collector current produces a greater voltage drop across the collector load resistance  $R_C$ . However, during the negative half-cycle of the

\* If d.c. bias voltage is not provided, then during negative half-cycle of the signal, the emitter-base junction will be reverse biased. This will upset the transistor action.

\*\* Throughout the book, we shall use sine wave signals because these are convenient for testing amplifiers. But it must be realised that signals (*e.g.* speech, music etc.) with which we work are generally complex having little resemblance to a sine wave. However, fourier series analysis tells us that such complex signals may be expressed as a sum of sine waves of various frequencies.

signal, the forward bias across emitter-base junction is decreased. Therefore, collector current decreases. This results in the decreased output voltage (in the opposite direction). Hence, an amplified output is obtained across the load.

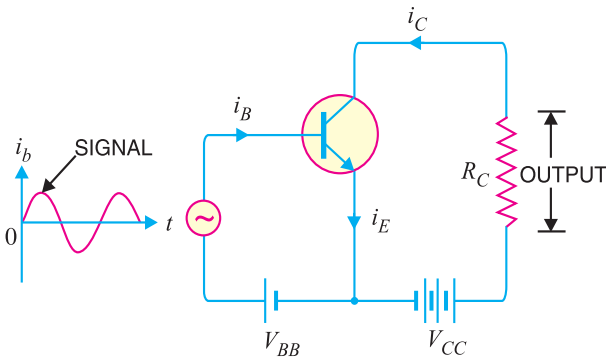


Fig. 8.33

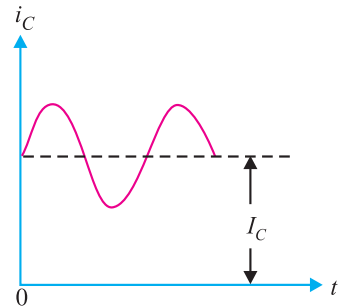


Fig. 8.34

**Analysis of collector currents.** When no signal is applied, the input circuit is forward biased by the battery  $V_{BB}$ . Therefore, a d.c. collector current  $I_C$  flows in the collector circuit. This is called *zero signal collector current*. When the signal voltage is applied, the forward bias on the emitter-base junction increases or decreases depending upon whether the signal is positive or negative. During the positive half-cycle of the signal, the forward bias on emitter-base junction is increased, causing total collector current  $i_C$  to increase. Reverse will happen for the negative half-cycle of the signal.

Fig. 8.34 shows the graph of total collector current  $i_C$  versus time. From the graph, it is clear that total collector current consists of two components, namely ;

(i) The d.c. collector current  $I_C$  (zero signal collector current) due to bias battery  $V_{BB}$ . This is the current that flows in the collector in the absence of signal.

(ii) The a.c. collector current  $i_c$  due to signal.

$$\therefore \text{Total collector current, } i_C = i_c + I_C$$

The useful output is the voltage drop across collector load  $R_C$  due to the a.c. component  $i_c$ . The purpose of zero signal collector current is to ensure that the emitter-base junction is forward biased at all times. The table below gives the symbols usually employed for currents and voltages in transistor applications.

S. No.	Particular	Instantaneous a.c.	d.c.	Total
1.	Emitter current	$i_e$	$I_E$	$i_E$
2.	Collector current	$i_c$	$I_C$	$i_C$
3.	Base current	$i_b$	$I_B$	$i_B$
4.	Collector-emitter voltage	$v_{ce}$	$V_{CE}$	$v_{CE}$
5.	Emitter-base voltage	$v_{eb}$	$V_{EB}$	$v_{EB}$

## 8.17 Transistor Load Line Analysis

In the transistor circuit analysis, it is generally required to determine the collector current for various collector-emitter voltages. One of the methods can be used to plot the output characteristics and determine the collector current at any desired collector-emitter voltage. However, a more convenient method, known as *load line method* can be used to solve such problems. As explained later in this section, this method is quite easy and is frequently used in the analysis of transistor applications.

**d.c. load line.** Consider a common emitter *npn* transistor circuit shown in Fig. 8.35 (i) where no signal is applied. Therefore, d.c. conditions prevail in the circuit. The output characteristics of this circuit are shown in Fig. 8.35 (ii).

The value of collector-emitter voltage  $V_{CE}$  at any time is given by ;

$$V_{CE} = V_{CC} - I_C R_C \quad \dots(i)$$

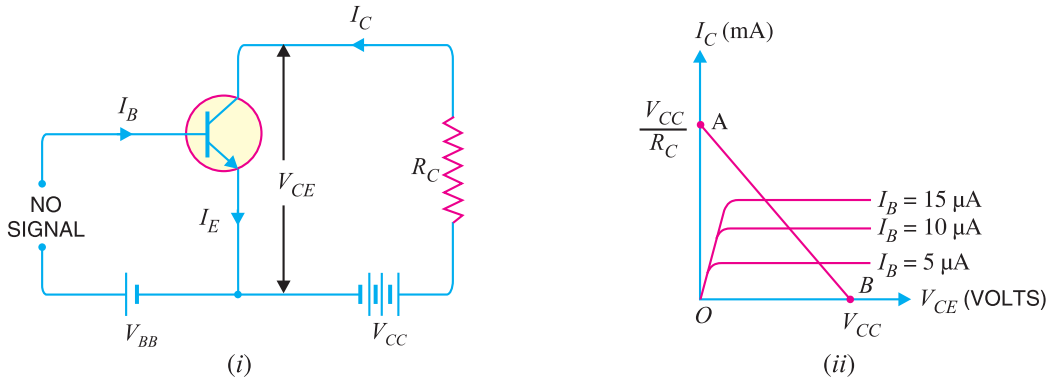


Fig. 8.35

As  $V_{CC}$  and  $R_C$  are fixed values, therefore, it is a first degree equation and can be represented by a straight line on the output characteristics. This is known as **d.c. load line** and determines the locus of  $V_{CE} - I_C$  points for any given value of  $R_C$ . To add load line, we need two end points of the straight line. These two points can be located as under :

(i) When the collector current  $I_C = 0$ , then collector-emitter voltage is maximum and is equal to  $V_{CC}$  i.e.

$$\begin{aligned} \text{Max. } V_{CE} &= V_{CC} - I_C R_C \\ &= V_{CC} \quad (\because I_C = 0) \end{aligned}$$

This gives the first point B ( $OB = V_{CC}$ ) on the collector-emitter voltage axis as shown in Fig. 8.35 (ii).

(ii) When collector-emitter voltage  $V_{CE} = 0$ , the collector current is maximum and is equal to  $V_{CC}/R_C$  i.e.

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ \text{or} \quad 0 &= V_{CC} - I_C R_C \\ \therefore \quad \text{Max. } I_C &= V_{CC}/R_C \end{aligned}$$

This gives the second point A ( $OA = V_{CC}/R_C$ ) on the collector current axis as shown in Fig. 8.35 (ii). By joining these two points, d.c. \*load line AB is constructed.

**Importance.** The current ( $I_C$ ) and voltage ( $V_{CE}$ ) conditions in the transistor circuit are represented by some point on the output characteristics. The same information can be obtained from the load line. Thus when  $I_C$  is maximum ( $= V_{CC}/R_C$ ), then  $V_{CE} = 0$  as shown in Fig. 8.36. If  $I_C = 0$ , then  $V_{CE}$  is maximum

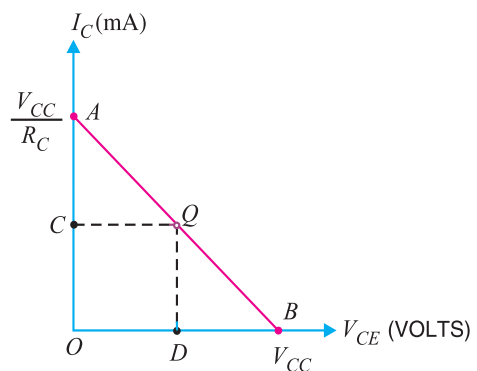


Fig. 8.36

\* **Why load line ?** The resistance  $R_C$  connected to the device is called load or load resistance for the circuit and, therefore, the line we have just constructed is called the load line.

and is equal to  $V_{CC}$ . For any other value of collector current say  $OC$ , the collector-emitter voltage  $V_{CE} = OD$ . It follows, therefore, that load line gives a far more convenient and direct solution to the problem.

**Note.** If we plot the load line on the output characteristic of the transistor, we can investigate the behaviour of the transistor amplifier. It is because we have the transistor output current and voltage specified in the form of load line equation and the transistor behaviour itself specified implicitly by the output characteristics.

## 8.18 Operating Point

The zero signal values of  $I_C$  and  $V_{CE}$  are known as the **operating point**.

It is called operating point because the variations of  $I_C$  and  $V_{CE}$  take place about this point when signal is applied. It is also called quiescent (silent) point or **Q-point** because it is the point on  $I_C - V_{CE}$  characteristic when the transistor is silent *i.e.* in the absence of the signal.

Suppose in the absence of signal, the base current is  $5 \mu\text{A}$ . Then  $I_C$  and  $V_{CE}$  conditions in the circuit must be represented by some point on  $I_B = 5 \mu\text{A}$  characteristic. But  $I_C$  and  $V_{CE}$  conditions in the circuit should also be represented by some point on the d.c. load line  $AB$ . The point  $Q$  where the load line and the characteristic intersect is the only point which satisfies both these conditions. Therefore, the point  $Q$  describes the actual state of affairs in the circuit in the zero signal conditions and is called the operating point. Referring to Fig. 8.37, for  $I_B = 5 \mu\text{A}$ , the zero signal values are :

$$\begin{aligned} V_{CE} &= OC \text{ volts} \\ I_C &= OD \text{ mA} \end{aligned}$$

It follows, therefore, that the zero signal values of  $I_C$  and  $V_{CE}$  (*i.e.* operating point) are determined by the point where d.c. load line intersects the proper base current curve.

**Example 8.22.** For the circuit shown in Fig. 8.38 (i), draw the d.c. load line.

**Solution.** The collector-emitter voltage  $V_{CE}$  is given by ;

$$V_{CE} = V_{CC} - I_C R_C \quad \dots(i)$$

When  $I_C = 0$ , then,

$$V_{CE} = V_{CC} = 12.5 \text{ V}$$

This locates the point  $B$  of the load line on the collector-emitter voltage axis.



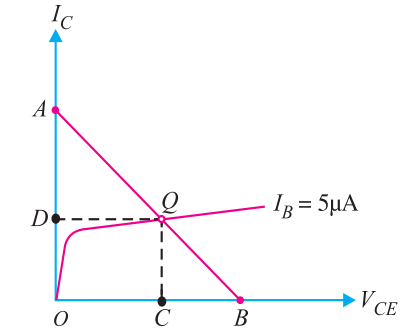


Fig. 8.37

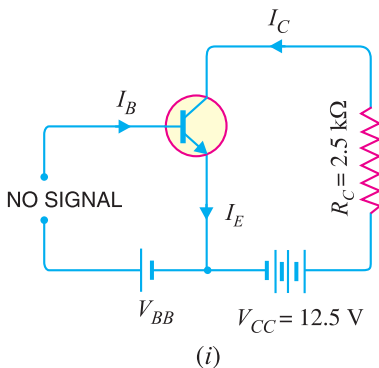

(ii)

Fig. 8.38

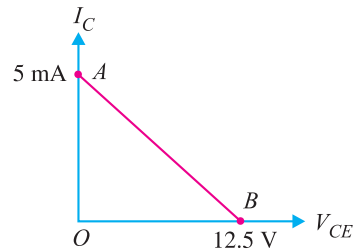

$$\text{When } V_{CE} = 0, \text{ then,} \\ I_C = V_{CC}/R_C = 12.5 \text{ V}/2.5 \text{ k}\Omega = 5 \text{ mA}$$

This locates the point A of the load line on the collector current axis. By joining these two points, we get the d.c. load line AB as shown in Fig. 8.38 (ii).

**Example 8.23.** In the circuit diagram shown in Fig. 8.39 (i), if  $V_{CC} = 12 \text{ V}$  and  $R_C = 6 \text{ k}\Omega$ , draw the d.c. load line. What will be the Q point if zero signal base current is  $20 \mu\text{A}$  and  $\beta = 50$ ?

**Solution.** The collector-emitter voltage  $V_{CE}$  is given by :



$$V_{CE} = V_{CC} - I_C R_C$$

When  $I_C = 0$ ,  $V_{CE} = V_{CC} = 12 \text{ V}$ . This locates the point B of the load line. When  $V_{CE} = 0$ ,  $I_C = V_{CC}/R_C = 12 \text{ V}/6 \text{ k}\Omega = 2 \text{ mA}$ . This locates the point A of the load line. By joining these two points, load line AB is constructed as shown in Fig. 8.39 (ii).

Zero signal base current,  $I_B = 20 \mu\text{A} = 0.02 \text{ mA}$

Current amplification factor,  $\beta = 50$

$\therefore$  Zero signal collector current,  $I_C = \beta I_B = 50 \times 0.02 = 1 \text{ mA}$

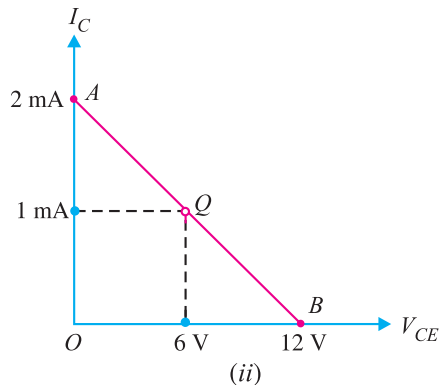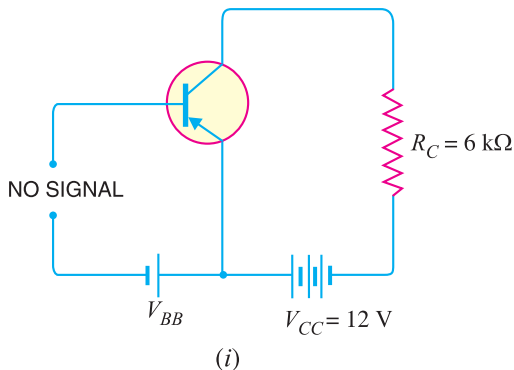

**Fig. 8.39**

Zero signal collector-emitter voltage is

$$V_{CE} = V_{CC} - I_C R_C = 12 - 1 \text{ mA} \times 6 \text{ k}\Omega = 6 \text{ V}$$

$\therefore$  Operating point is **6 V, 1 mA**.

Fig. 8.39 (ii) shows the Q point. Its co-ordinates are  $I_C = 1 \text{ mA}$  and  $V_{CE} = 6 \text{ V}$ .

**Example 8.24.** In a transistor circuit, collector load is  $4 \text{ k}\Omega$  whereas quiescent current (zero signal collector current) is  $1 \text{ mA}$ .

(i) What is the operating point if  $V_{CC} = 10 \text{ V}$ ?

(ii) What will be the operating point if  $R_C = 5 \text{ k}\Omega$ ?

**Solution.**

$$V_{CC} = 10 \text{ V}, I_C = 1 \text{ mA}$$

(i) When collector load  $R_C = 4 \text{ k}\Omega$ , then,

$$V_{CE} = V_{CC} - I_C R_C = 10 - 1 \text{ mA} \times 4 \text{ k}\Omega = 10 - 4 = 6 \text{ V}$$

$\therefore$  Operating point is **6 V, 1 mA**.

(ii) When collector load  $R_C = 5 \text{ k}\Omega$ , then,

$$V_{CE} = V_{CC} - I_C R_C = 10 - 1 \text{ mA} \times 5 \text{ k}\Omega = 10 - 5 = 5 \text{ V}$$

$\therefore$  Operating point is **5 V, 1 mA**.

**Example 8.25.** Determine the Q point of the transistor circuit shown in Fig. 8.40. Also draw the d.c. load line. Given  $\beta = 200$  and  $V_{BE} = 0.7 \text{ V}$ .

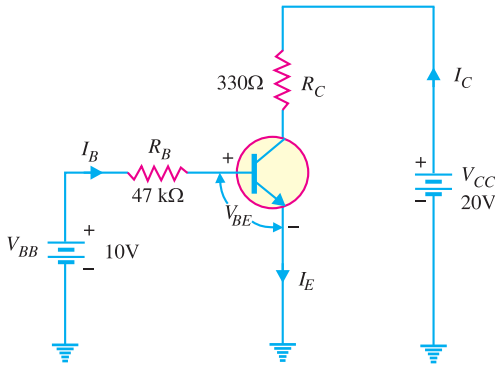


Fig. 8.40

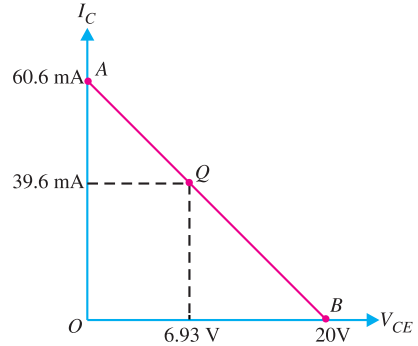


Fig. 8.41

**Solution.** The presence of resistor  $R_B$  in the base circuit should not disturb you because we can apply Kirchhoff's voltage law to find the value of  $I_B$  and hence  $I_C (= \beta I_B)$ . Referring to Fig. 8.40 and applying Kirchhoff's voltage law to base-emitter loop, we have,

$$V_{BB} - I_B R_B - V_{BE} = 0$$

$$\therefore I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{10V - 0.7V}{47 \text{ k}\Omega} = 198 \mu\text{A}$$

$$\text{Now } I_C = \beta I_B = (200)(198 \mu\text{A}) = 39.6 \text{ mA}$$

$$\text{Also } V_{CE} = V_{CC} - I_C R_C = 20V - (39.6 \text{ mA})(330 \Omega) = 20V - 13.07V = 6.93V$$

Therefore, the Q-point is  $I_C = \mathbf{39.6 \text{ mA}}$  and  $V_{CE} = \mathbf{6.93V}$ .

**D.C. load line.** In order to draw the d.c. load line, we need two end points.

$$V_{CE} = V_{CC} - I_C R_C$$

When  $I_C = 0$ ,  $V_{CE} = V_{CC} = 20V$ . This locates the point B of the load line on the collector-emitter voltage axis as shown in Fig. 8.41. When  $V_{CE} = 0$ ,  $I_C = V_{CC}/R_C = 20V/330\Omega = 60.6 \text{ mA}$ . This locates the point A of the load line on the collector current axis. By joining these two points, d.c. load line AB is constructed as shown in Fig. 8.41.

**Example 8.26.** Determine the Q point of the transistor circuit shown in \*Fig. 8.42. Also draw the d.c. load line. Given  $\beta = 100$  and  $V_{BE} = 0.7V$ .

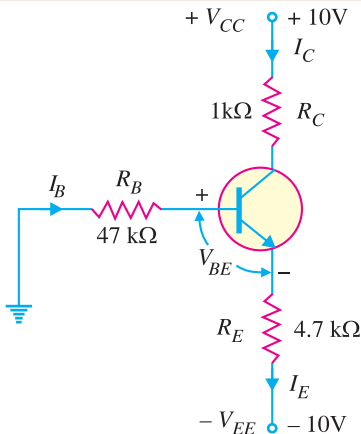


Fig. 8.42

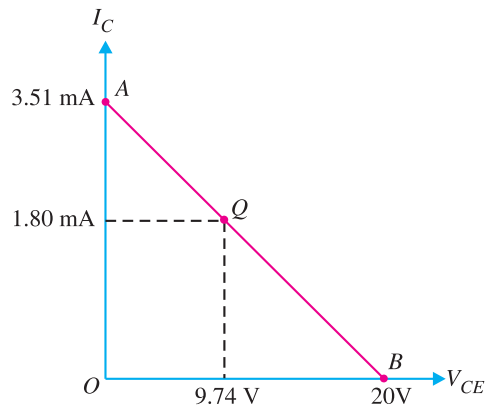


Fig. 8.43

\* The presence of two power supplies has an effect on the basic equations for  $I_C$  and  $V_{CE}$  used for single power supply (i.e.  $V_{CC}$ ). Normally, the two supply voltages will be equal. For example, if  $V_{CC} = +10V$  (d.c.), then  $V_{EE} = -10V$  (d.c.).

## 170 ■ Principles of Electronics

**Solution.** The transistor circuit shown in Fig. 8.42 may look complex but we can easily apply Kirchhoff's voltage law to find the various voltages and currents in the \* circuit.

Applying Kirchhoff's voltage law to the base-emitter loop, we have,

$$-I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0 \quad \text{or} \quad V_{EE} = I_B R_B + I_E R_E + V_{BE}$$

Now  $I_C = \beta I_B$  and  $I_C \simeq I_E$ .  $\therefore I_B = I_E / \beta$ . Putting  $I_B = I_E / \beta$  in the above equation, we have,

$$V_{EE} = \left( \frac{I_E}{\beta} \right) R_B + I_E R_E + V_{BE}$$

$$\text{or} \quad I_E \left( \frac{R_B}{\beta} + R_E \right) = V_{EE} - V_{BE} \quad \text{or} \quad I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta}$$

$$\text{Since } I_C \simeq I_E, \quad I_C = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta} = \frac{10\text{V} - 0.7\text{V}}{4.7 \text{ k}\Omega + 47 \text{ k}\Omega / 100} = \frac{9.3 \text{ V}}{5.17 \text{ k}\Omega} = 1.8 \text{ mA}$$

Applying Kirchhoff's voltage law to the collector side, we have,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E + V_{EE} = 0$$

$$\begin{aligned} \text{or} \quad V_{CE} &= V_{CC} + V_{EE} - I_C (R_C + R_E) & (\text{Q } I_E \simeq I_C) \\ &= 10\text{V} + 10\text{V} - 1.8 \text{ mA} (1 \text{ k}\Omega + 4.7 \text{ k}\Omega) = 9.74\text{V} \end{aligned}$$

Therefore, the operating point of the circuit is  $I_C = 1.8 \text{ mA}$  and  $V_{CE} = 9.74\text{V}$ .

**D.C. load line.** The d.c. load line can be constructed as under :


$$V_{CE} = V_{CC} + V_{EE} - I_C (R_C + R_E)$$

When  $I_C = 0$ ;  $V_{CE} = V_{CC} + V_{EE} = 10\text{V} + 10\text{V} = 20\text{V}$ . This locates the first point B ( $OB = 20\text{V}$ ) of the load line on the collector-emitter voltage axis. When  $V_{CE} = 0$ ,

$$I_C = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{10\text{V} + 10\text{V}}{1 \text{ k}\Omega + 4.7 \text{ k}\Omega} = \frac{20\text{V}}{5.7 \text{ k}\Omega} = 3.51 \text{ mA}$$

This locates the second point A ( $OA = 3.51 \text{ mA}$ ) of the load line on the collector current axis. By joining points A and B, d.c. load line AB is constructed as shown in Fig. 8.43.

**Example 8.27.** In the above example, find (i) emitter voltage w.r.t. ground (ii) base voltage w.r.t. ground (iii) collector voltage w.r.t. ground.

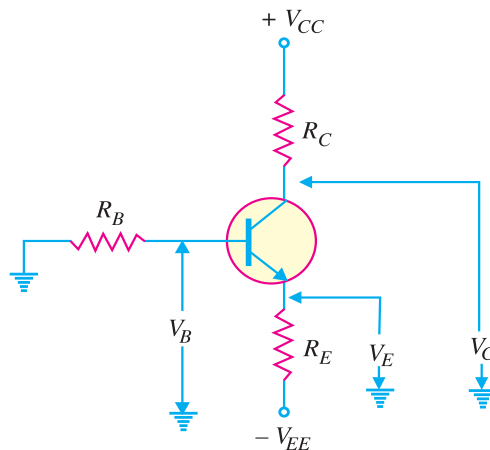

**Fig. 8.44**

\* The emitter resistor  $R_E$  provides stabilisation of Q-point (See Art. 9.12).

$$\begin{aligned}\Delta V_{BE} &= 200 \text{ mV} \\ \text{Change in base current, } \Delta I_B &= 100 \text{ } \mu\text{A} \\ \therefore \text{Input resistance, } R_i &= \frac{\Delta V_{BE}}{\Delta I_B} = \frac{200 \text{ mV}}{100 \text{ } \mu\text{A}} = \mathbf{2 \text{ k}\Omega}\end{aligned}$$

**Example 8.29.** If the collector current changes from 2 mA to 3mA in a transistor when collector-emitter voltage is increased from 2V to 10V, what is the output resistance ?

**Solution.** Change in collector-emitter voltage is

$$\begin{aligned}\Delta V_{CE} &= 10 - 2 = 8 \text{ V} \\ \text{Change in collector current is } \Delta I_C &= 3 - 2 = 1 \text{ mA} \\ \therefore \text{Output resistance, } R_o &= \frac{\Delta V_{CE}}{\Delta I_C} = \frac{8 \text{ V}}{1 \text{ mA}} = \mathbf{8 \text{ k}\Omega}\end{aligned}$$

**Example 8.30.** For a single stage transistor amplifier, the collector load is  $R_C = 2\text{k}\Omega$  and the input resistance  $R_i = 1\text{k}\Omega$ . If the current gain is 50, calculate the voltage gain of the amplifier.

**Solution.** Collector load,  $R_C = 2 \text{ k}\Omega$

Input resistance,  $R_i = 1 \text{ k}\Omega$

Current gain,  $\beta = 50$



$$\begin{aligned}\therefore \text{Voltage gain, } A_v &= \beta \times \frac{R_{AC}}{R_i} = \beta \times \frac{R_C}{R_i} \quad [\because \text{For single stage, } R_{AC} = R_C] \\ &= 50 \times (2/1) = \mathbf{100}\end{aligned}$$

## 8.22 Cut off and Saturation Points

Fig. 8.49 (i) shows CE transistor circuit while Fig. 8.49 (ii) shows the output characteristics along with the d.c. load line.

(i) **Cut off.** The point where the load line intersects the  $I_B = 0$  curve is known as **cut off**. At this point,  $I_B = 0$  and only small collector current (i.e. collector leakage current  $I_{CEO}$ ) exists. At cut off, the base-emitter junction no longer remains forward biased and normal transistor action is lost. The collector-emitter voltage is nearly equal to  $V_{CC}$  i.e.

$$V_{CE(\text{cut off})} = V_{CC}$$

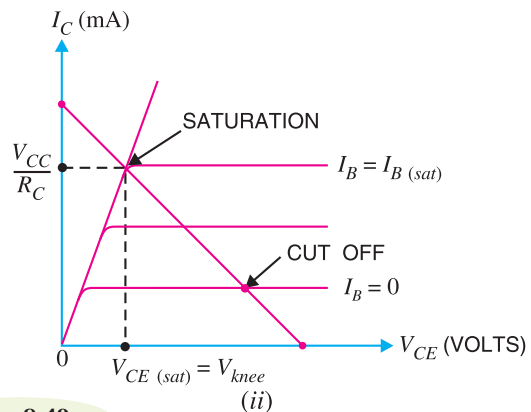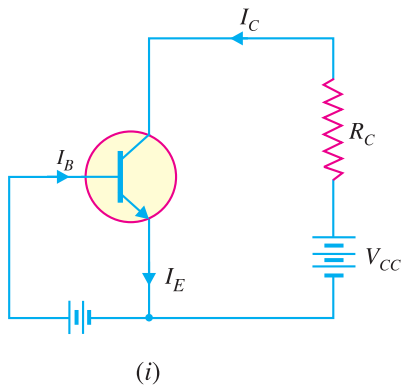

**Fig. 8.49**

(ii) **Saturation.** The point where the load line intersects the  $I_B = I_{B(sat)}$  curve is called **saturation**. At this point, the base current is maximum and so is the collector current. At saturation, collector-base junction no longer remains reverse biased and normal transistor action is lost.

$$I_{C(sat)} \simeq \frac{V_{CC}}{R_C}; \quad V_{CE} = V_{CE(sat)} = V_{knee}$$

If base current is greater than  $I_{B(sat)}$ , then collector current cannot increase because collector-base junction is no longer reverse-biased.

**(iii) Active region.** The region between cut off and saturation is known as **active region**. In the active region, collector-base junction remains reverse biased while base-emitter junction remains forward biased. Consequently, the transistor will function normally in this region.

**Note.** We provide biasing to the transistor to ensure that it operates in the active region. The reader may find the detailed discussion on transistor biasing in the next chapter.

**Summary.** A transistor has two *pn* junctions *i.e.*, it is like two diodes. The junction between base and emitter may be called **emitter diode**. The junction between base and collector may be called **collector diode**. We have seen above that transistor can act in one of the three states : **cut-off**, **saturated** and **active**. The state of a transistor is entirely determined by the states of the emitter diode and collector diode [See Fig. 8.50]. The relations between the diode states and the transistor states are :

**CUT-OFF :** Emitter diode and collector diode are **OFF**.

**ACTIVE :** Emitter diode is **ON** and collector diode is **OFF**.

**SATURATED :** Emitter diode and collector diode are **ON**.

In the **active state**, collector current [See Fig 8.51 (i)] is  $\beta$  times the base current (*i.e.*  $I_C = \beta I_B$ ). If the transistor is **cut-off**, there is no base current, so there is no collector or emitter current. That is collector emitter pathway is open [See Fig. 8.51 (ii)]. In **saturation**, the collector and emitter are, in effect, shorted together. That is the transistor behaves as though a switch has been closed between the collector and emitter [See Fig. 8.51 (iii)].

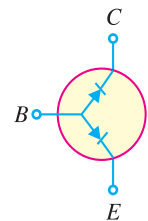


Fig. 8.50

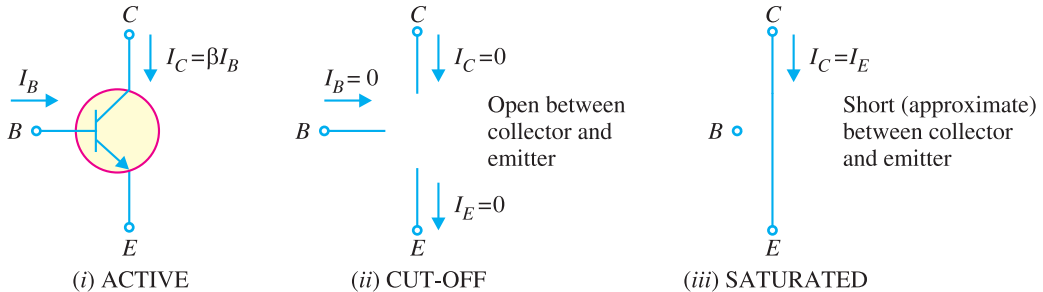


Fig. 8.51

**Note.** When the transistor is in the active state,  $I_C = \beta I_B$ . Therefore, a transistor acts as an amplifier when operating in the active state. Amplification means **linear amplification**. In fact, small signal amplifiers are the most common **linear devices**.

**Example 8.31.** Find  $I_{C(sat)}$  and  $V_{CE(cut\ off)}$  for the circuit shown in Fig. 8.52 (i).

**Solution.** As we decrease  $R_B$ , base current and hence collector current increases. The increased collector current causes a greater voltage drop across  $R_C$ ; this decreases the collector-emitter voltage. Eventually at some value of  $R_B$ ,  $V_{CE}$  decreases to  $V_{knee}$ . At this point, collector-base junction is no longer reverse biased and transistor action is lost. Consequently, further increase in collector current is not possible. The transistor conducts maximum collector current ; we say the transistor is saturated.


$$I_{C(sat)} = \frac{V_{CC} - V_{knee}}{R_C} = \frac{V_{CC}}{R_C} = \frac{20\text{ V}}{1\text{ k}\Omega} = 20\text{ mA}$$

\*  $V_{knee}$  is about 0.5 V for Ge transistor and about 1V for Si transistor. Consequently,  $V_{knee}$  can be neglected as compared to  $V_{CC}$  (= 20 V in this case).

## 176 ■ Principles of Electronics

As we increase  $R_B$ , base current and hence collector current decreases. This decreases the voltage drop across  $R_C$ . This increases the collector-emitter voltage. Eventually, when  $I_B = 0$ , the emitter-base junction is no longer forward biased and transistor action is lost. Consequently, further increase in  $V_{CE}$  is not possible. In fact,  $V_{CE}$  now equals to  $V_{CC}$ .

$$V_{CE(\text{cut-off})} = V_{CC} = 20 \text{ V}$$

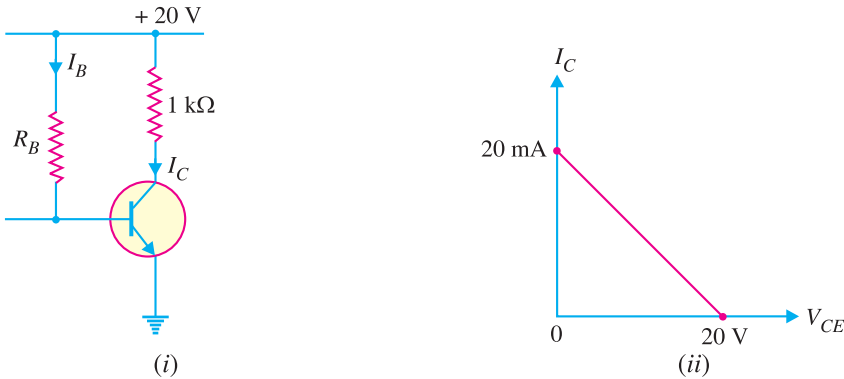


**Fig. 8.52**

Figure 8.52 (ii) shows the saturation and cut off points. Incidentally, they are end points of the d.c. load line.

**Note.** The exact value of  $V_{CE(\text{cut-off})} = V_{CC} - I_{CEO} R_C$ . Since the collector leakage current  $I_{CEO}$  is very small, we can neglect  $I_{CEO} R_C$  as compared to  $V_{CC}$ .

**Example 8.32.** Determine the values of  $V_{CE(\text{off})}$  and  $I_{C(\text{sat})}$  for the circuit shown in Fig. 8.53.

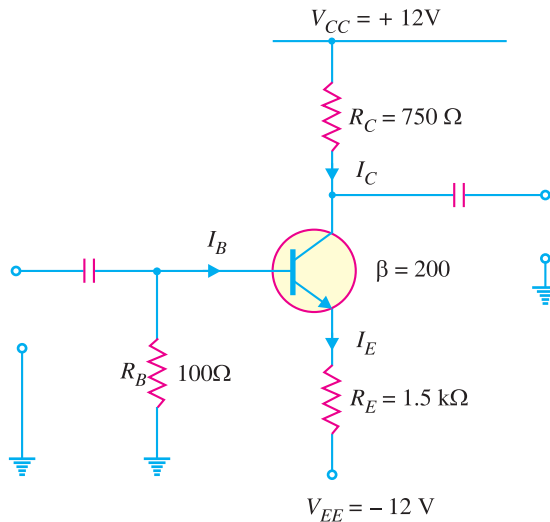

**Fig. 8.53**

**Solution.** Applying Kirchhoff's voltage law to the collector side of the circuit in Fig. 8.53, we have,

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E + V_{EE} = 0$$

$$\text{or } V_{CE} = V_{CC} + V_{EE} - I_C (R_C + R_E) \quad \dots (i)$$

\* Voltage across  $R_E = I_E R_E$ . Since  $I_E \approx I_C$ , voltage across  $R_E = I_C R_E$ .

We have  $V_{CE(off)}$  when  $I_C = 0$ . Therefore, putting  $I_C = 0$  in eq. (i), we have,

$$V_{CE(off)} = V_{CC} + V_{EE} = 12 + 12 = \mathbf{24V}$$

We have  $I_{C(sat)}$  when  $V_{CE} = 0$ .

$$\therefore I_{C(sat)} = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{(12 + 12)V}{(750 + 1500)\Omega} = \mathbf{10.67\text{ mA}}$$

**Example 8.33.** Determine whether or not the transistor in Fig. 8.54 is in saturation. Assume  $V_{knee} = 0.2V$ .

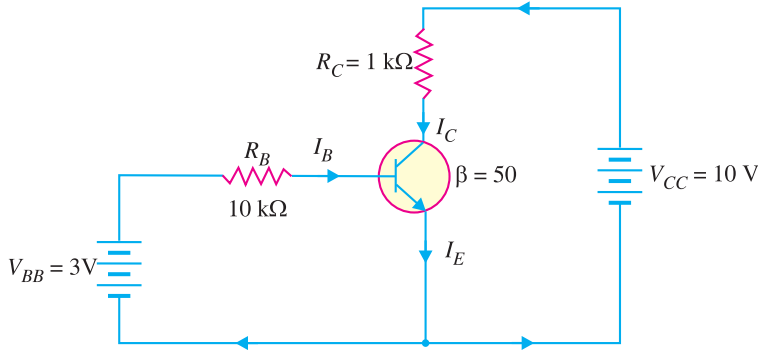


Fig. 8.54

**Solution.**

$$I_{C(sat)} = \frac{V_{CC} - V_{knee}}{R_C} = \frac{10V - 0.2V}{1\text{ k}\Omega} = \frac{9.8V}{1\text{ k}\Omega} = 9.8\text{ mA}$$

Now we shall see if  $I_B$  is large enough to produce  $I_{C(sat)}$ .

$$\text{Now } I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3V - 0.7V}{10\text{ k}\Omega} = \frac{2.3V}{10\text{ k}\Omega} = 0.23\text{ mA}$$

$$\therefore I_C = \beta I_B = 50 \times 0.23 = 11.5\text{ mA}$$

This shows that with specified  $\beta$ , this base current ( $= 0.23\text{ mA}$ ) is capable of producing  $I_C$  greater than  $I_{C(sat)}$ . Therefore, the transistor is **saturated**. In fact, the collector current value of  $11.5\text{ mA}$  is never reached. If the base current value corresponding to  $I_{C(sat)}$  is increased, the collector current remains at the saturated value ( $= 9.8\text{ mA}$ ).

**Example 8.34.** Is the transistor in Fig. 8.55 operating in saturated state ?

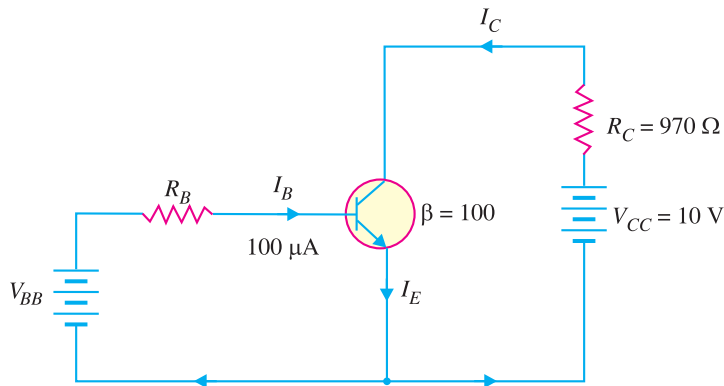



Fig. 8.55

**Solution.**

$$\begin{aligned}
 I_C &= \beta I_B = (100)(100 \mu\text{A}) = 10 \text{ mA} \\
 V_{CE} &= V_{CC} - I_C R_C \\
 &= 10\text{V} - (10 \text{ mA})(970\Omega) = 0.3\text{V}
 \end{aligned}$$

Let us relate the values found to the transistor shown in Fig. 8.56. As you can see, the value of  $V_{BE}$  is 0.95V and the value of  $V_{CE} = 0.3\text{V}$ . This leaves  $V_{CB}$  of 0.65V (Note that  $V_{CE} = V_{CB} + V_{BE}$ ). In this case, collector – base junction (*i.e.*, collector diode) is forward biased as is the emitter-base junction (*i.e.*, emitter diode). Therefore, the transistor is operating in the **saturation region**.

**Note.** When the transistor is in the saturated state, the base current and collector current are independent of each other. The base current is still (and always is) found only from the base circuit. The collector current is found approximately by closing the imaginary switch between the collector and the emitter in the collector circuit.

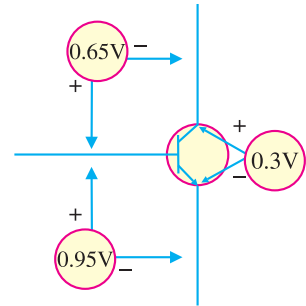**Fig. 8.56**

**Example 8.35.** For the circuit in Fig. 8.57, find the base supply voltage ( $V_{BB}$ ) that just puts the transistor into saturation. Assume  $\beta = 200$ .

**Solution.** When transistor first goes into saturation, we can assume that the collector shorts to the emitter (*i.e.*  $V_{CE} = 0$ ) but the collector current is still  $\beta$  times the base current.

$$\begin{aligned}
 I_{C(sat)} &= \frac{V_{CC} - V_{CE}}{R_C} = \frac{V_{CC} - 0}{R_C} \\
 &= \frac{10\text{V} - 0}{2 \text{ k}\Omega} = 5 \text{ mA}
 \end{aligned}$$

The base current  $I_B$  corresponding to  $I_{C(sat)} (= 5 \text{ mA})$  is

$$I_B = \frac{I_{C(sat)}}{\beta} = \frac{5 \text{ mA}}{200} = 0.025 \text{ mA}$$

Applying Kirchhoff's voltage law to the base circuit, we have,

$$\begin{aligned}
 V_{BB} - I_B R_B - V_{BE} &= 0 \\
 \text{or } V_{BB} &= V_{BE} + I_B R_B \\
 &= 0.7\text{V} + 0.025 \text{ mA} \times 50 \text{ k}\Omega = 0.7 + 1.25 = 1.95\text{V}
 \end{aligned}$$

Therefore, for  $V_{BB} \geq 1.95$ , the transistor will be in **saturation**.

**Example 8.36.** Determine the state of the transistor in Fig. 8.58 for the following values of collector resistor :

- (i)  $R_C = 2 \text{ k}\Omega$  (ii)  $R_C = 4 \text{ k}\Omega$  (iii)  $R_C = 8 \text{ k}\Omega$

**Solution.** Since  $I_E$  does not depend on the value of the collector resistor  $R_C$ , the emitter current ( $I_E$ ) is the same for all three parts.


$$\begin{aligned}
 \text{Emitter voltage, } V_E &= V_B - V_{BE} = V_{BB} - V_{BE} \\
 &= 2.7\text{V} - 0.7 \text{ V} = 2\text{V}
 \end{aligned}$$

$$\text{Also } I_E = \frac{V_E}{R_E} = \frac{2\text{V}}{1 \text{ k}\Omega} = 2 \text{ mA}$$

- (i) **When  $R_C = 2 \text{ k}\Omega$ .** Suppose the transistor is active.

$$\therefore I_C = I_E = 2 \text{ mA}$$

$$\therefore I_B = I_C / \beta = 2 \text{ mA} / 100 = 0.02 \text{ mA}$$

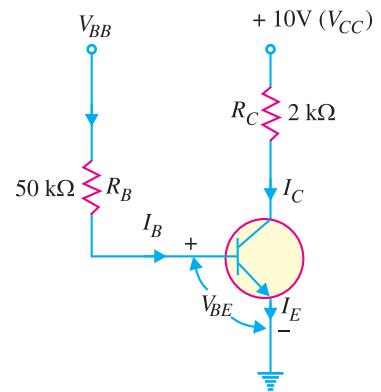**Fig. 8.57**